

```
1 {
2    'nombre': 'Barrera Peña Víctor Miguel',
3    'tipo': 'Tarea',
4    'no': '35',
5    'grupo': '6',
6    'materia': '1645 Diseño Digital Moderno',
7    'semestre': '2022-1',
8    'enunciado': 'Minimizar la función de 7 segmentos ',
9    'fecha': '15-10-2021'
```

Minimizar la función de 7 segmentos

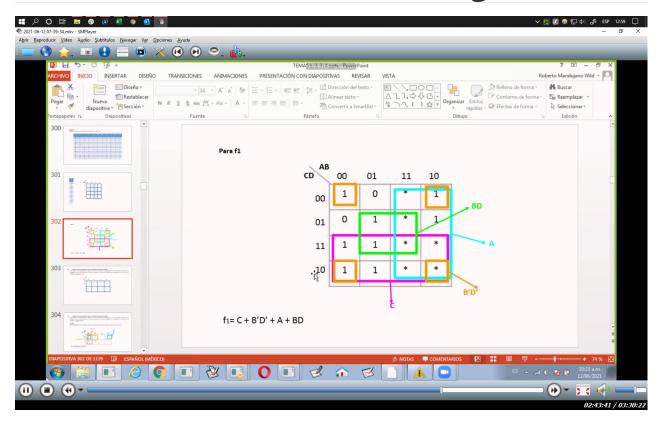

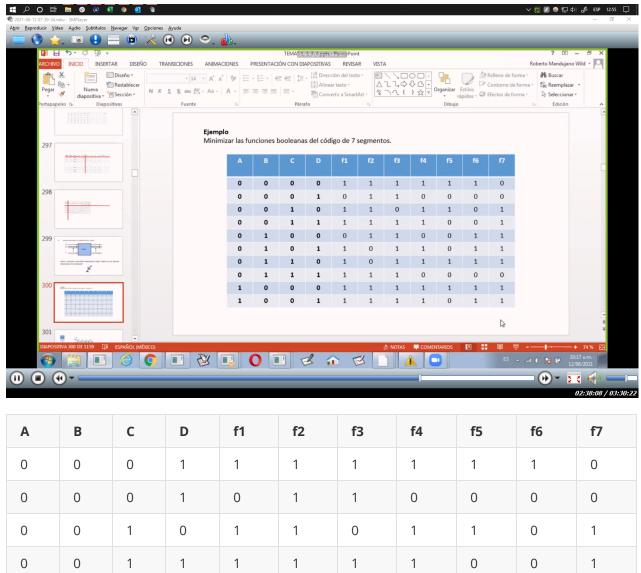



La tabla donde dibujar

	00	01	11	10
00	1	0	*	1
01	0	1	*	1
11	1	1	*	*
10	1	1	*	*

	00	01	11	10
00	1	1	*	1
01	1	0	*	1
11	1	1	*	*
10	1	0	*	*

f3

	00	01	11	10
00	1	1	*	1
01	1	1	*	1
11	1	1	*	*
10	0	1	*	*

f4

	00	01	11	10
00	1	0	*	1
01	0	1	*	1
11	1	1	*	*
10	1	0	*	*

	00	01	11	10
00	1	0	*	1
01	0	0	*	0
11	0	0	*	*
10	1	1	*	*

	00	01	11	10
00	1	1	*	1
01	0	1	*	1
11	0	0	*	*
10	0	1	*	*

f7

	00	01	11	10
00	0	1	*	1
01	0	1	*	1
11	1	0	*	*
10	1	1	*	*

Minimizando las funciones

